

디지털시스템입문

# Solutions to Final Exam

# Problem 1 [20 points]

Given  $X = (1101010)_2$  and  $Y = (0101011)_2$ , (a) find  $X - Y$ , and (b) find  $Y - X$  using 1's complements.

1-(a)

$$X - Y = 1101010 - 0101011$$

$$\begin{array}{r} 1101010 \quad (= X) \\ + 1010100 \quad (= 1's \text{ complement of } Y) \\ \hline \end{array}$$

$$1\ 0111110 \quad (= \text{Sum})$$

$$\begin{array}{r} 0111110 \\ + \quad 1 \quad (= \text{End-around carry}) \\ \hline \end{array}$$

$$= 0111111 \quad (= \text{Answer})$$

1-(b)

$$Y - X = 0101011 - 1101010$$

$$\begin{array}{r} 0101011 \\ + 0010101 \quad (= 1's \text{ complement of } X) \\ \hline \end{array}$$

$$1000000 \quad (= \text{Sum})$$


There is no end-carry. Therefore, the answer is  
 $Y - X = -(1's \text{ complement of } 1000000)$   
 $= -0111111$

# Problem 2 [20 points]

(a) By using K-maps, simplify the Boolean function  $F(w, x, y, z) = \Sigma(4, 5, 6, 7, 12)$  with don't-care function  $d(w, x, y, z) = \Sigma(0, 8, 13)$ , and (b) draw the logic diagram of the simplified Boolean function  $F$ .

2-(a)

wxyz	F
0000	X
0001	0
0010	0
0011	0
0100	1
0101	1
0110	1
0111	1
1000	X
1001	0
1010	0
1011	0
1100	1
1101	X
1110	0
1111	0


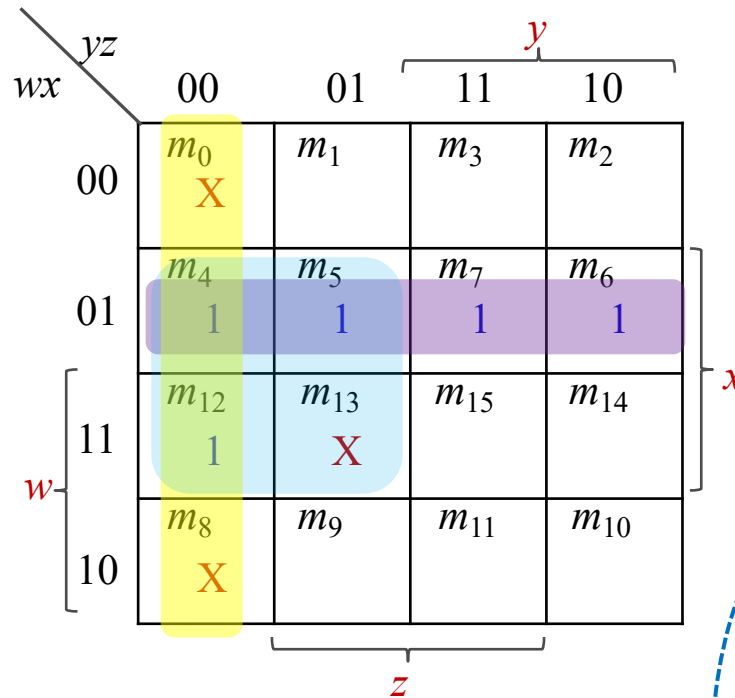


$$F(w, x, y, z) = w'x + y'z'$$

or

$$F(w, x, y, z) = w'x + xy'$$

2-(b)

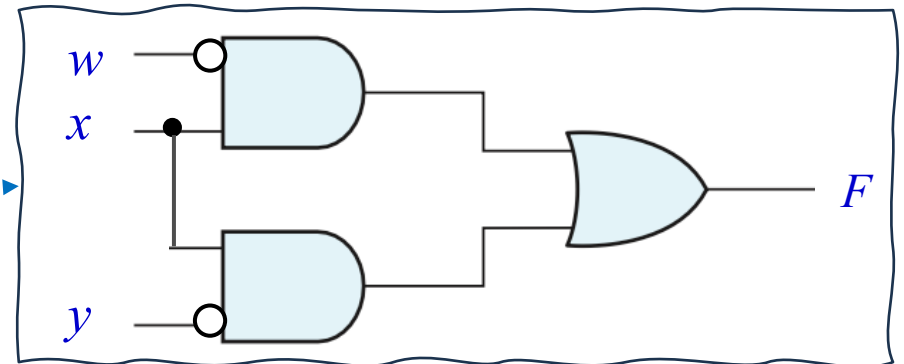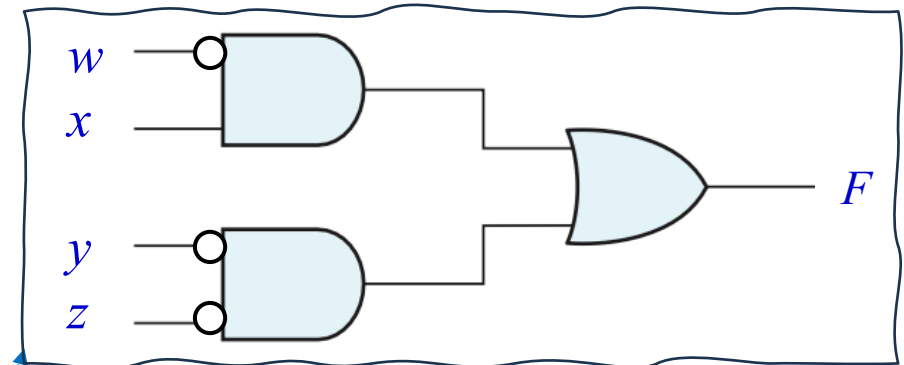

# Problem 3 [30 points] (1/4)

Using  $JK$  flip-flops,

- (a) Design a counter with the following repeated binary sequence: 0, 1, 2, 3, 4, 5, 6.
- (b) Draw the state transition diagram of the counter.
- (c) Draw the logic diagram of the counter.

## 3-(a) State table

Present State	Next state	Flip-flop inputs					
$ABC$	$ABC$	$J_A$	$K_A$	$J_B$	$K_B$	$J_C$	$K_C$
000	001	0	X	0	X	1	X
001	010	0	X	1	X	X	1
010	011	0	X	X	0	1	X
011	100	1	X	X	1	X	1
100	101	X	0	0	X	1	X
101	110	X	0	1	X	X	1
110	000	X	1	X	1	0	X
111	XXX	X	X	X	X	X	X

Excitation Table

$Q(t)$	$Q(t+1)$	$J$	$K$
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

(a)  $JK$  Flip-Flop



# Problem 3 (2/4)

## 3-(a) K-Maps

The simplified flip-flop input equations driven from K-maps are:

$$J_A = BC$$

$$K_A = B$$

$$J_B = C$$

$$K_B = A + C$$

$$J_C = A' + B'$$

$$K_C = 1$$

		B			
		00	01	11	10
A	0	$m_0$	$m_1$	$m_3$	$m_2$
	1	$m_4$	$m_5$	$m_7$	$m_6$
				1	
		x	x	x	x

$$J_A = BC$$

		B			
		00	01	11	10
A	0	$m_0$	$m_1$	$m_3$	$m_2$
	1	$m_4$	$m_5$	$m_7$	$m_6$
		x	x	x	x
				x	1

$$K_A = B$$

		B			
		00	01	11	10
A	0	$m_0$	$m_1$	$m_3$	$m_2$
	1	$m_4$	$m_5$	$m_7$	$m_6$
			1	x	x
			1	x	x

$$J_B = C$$

		B			
		00	01	11	10
A	0	$m_0$	$m_1$	$m_3$	$m_2$
	1	$m_4$	$m_5$	$m_7$	$m_6$
		x	x	1	
		x	x	x	1

$$K_B = A + C$$

		B			
		00	01	11	10
A	0	$m_0$	$m_1$	$m_3$	$m_2$
	1	$m_4$	$m_5$	$m_7$	$m_6$
		1	x	x	1
		1	x	x	


$$J_C = A' + B'$$

		B			
		00	01	11	10
A	0	$m_0$	$m_1$	$m_3$	$m_2$
	1	$m_4$	$m_5$	$m_7$	$m_6$
		x	1	1	x
		x	1	x	x

$$K_C = 1$$

# Problem 3 (3/4)

## 3-(b) State transition diagram

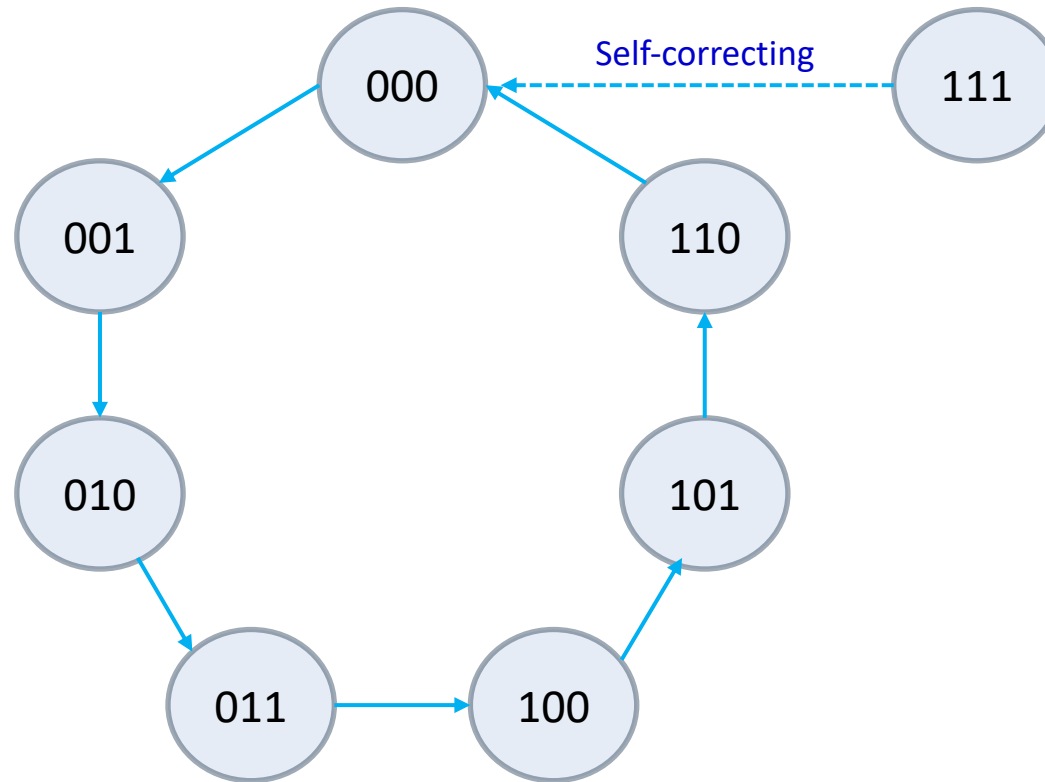

# Problem 3 (4/4)

## 3-(c) Logic circuit diagram

$$J_A = BC$$


$$K_A = B$$

$$J_B = C$$

$$K_B = A + C$$

$$J_C = A' + B'$$


$$K_C = 1$$

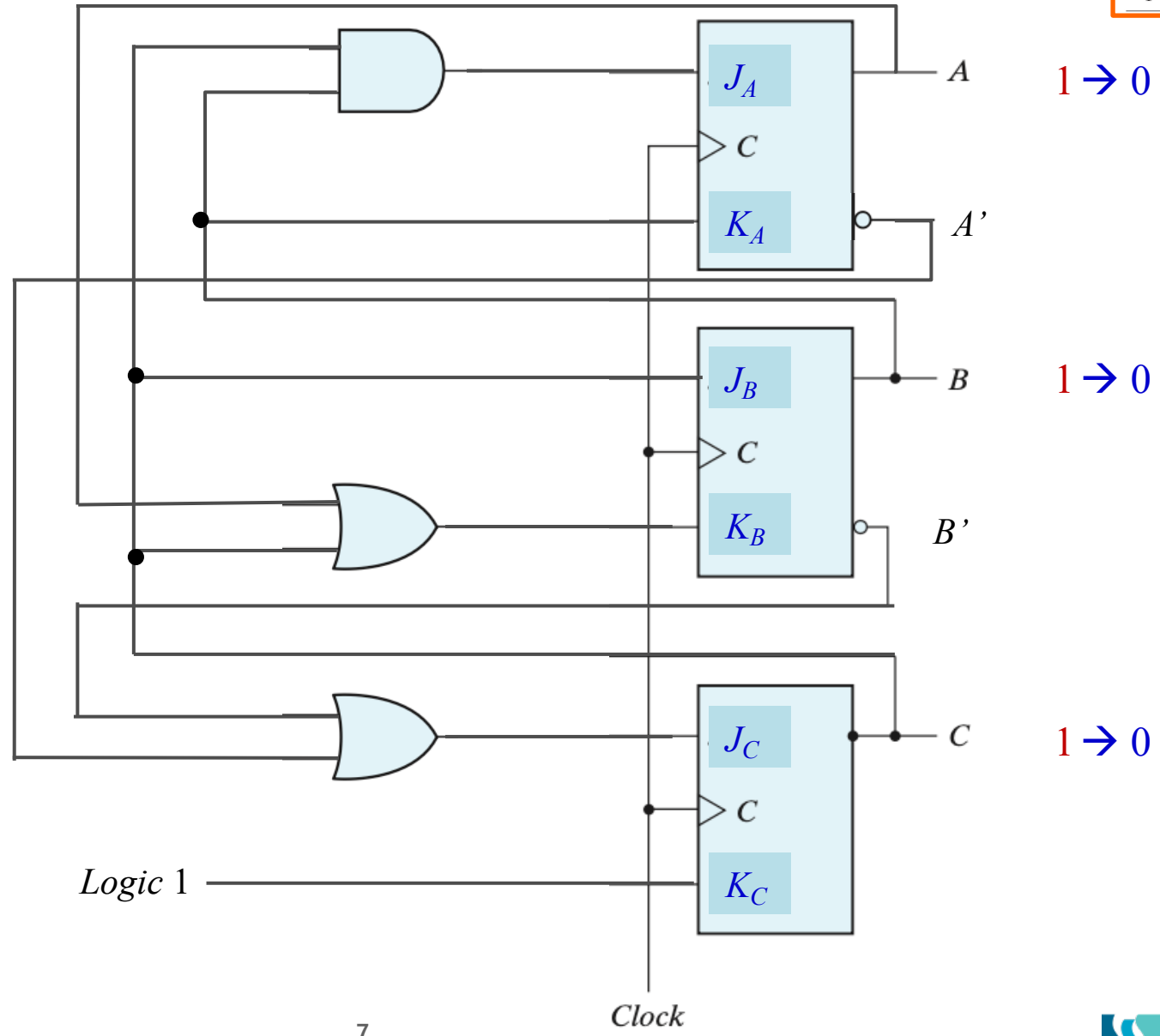

JK Flip-Flop			
J	K	Q(t + 1)	
0	0	Q(t)	No change
0	1	0	Reset
1	0	1	Set
1	1	Q'(t)	Complement

# Problem 4 [30 points]

Problem 4 is defined for yourself.

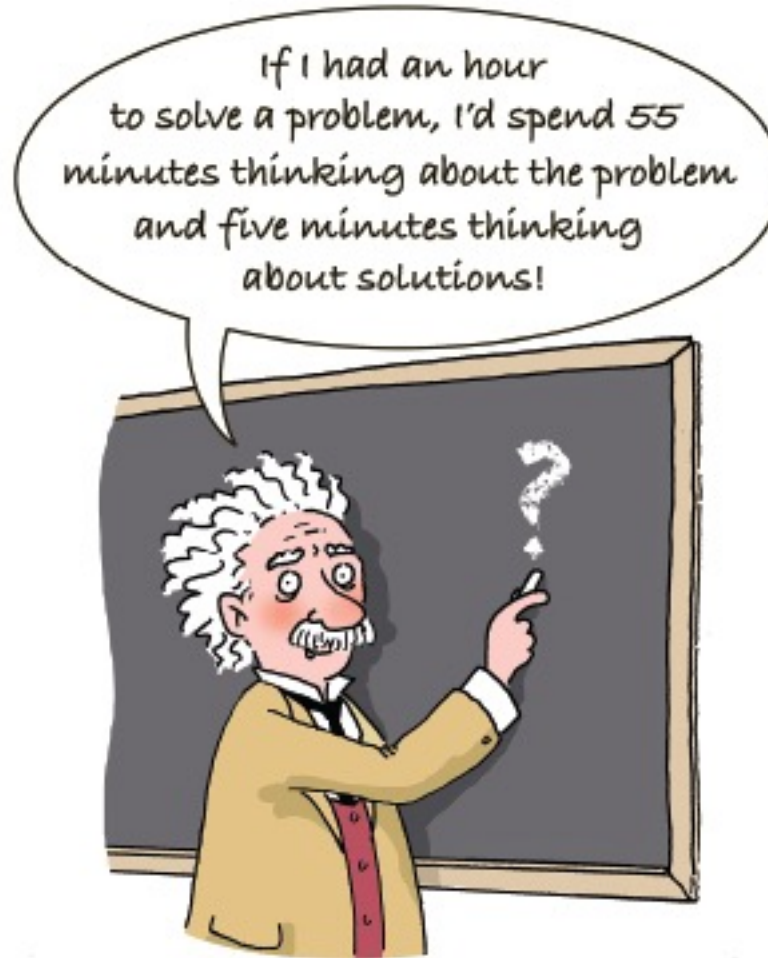

<https://www.open.edu/openlearncreate/mod/oucontent/view.php?id=80245&printable=1>



