

Engaged Learning Practice

#1

Application of Voltage Divider (Chap. 4)

Suppose your supervisor has given you a **voltage divider board to evaluate and modify** if necessary.


You will use it to obtain **five different voltage levels** from a 12 V battery that has a 6.5 Ah rating. The **voltage divider provides positive reference voltages** to an electronic circuit in an analog-to-digital converter.

- Your job will be to **check the circuit** to see if it provides the following voltages within a tolerance of $\pm 5\%$ with respect to the negative side of the battery: **10.4 V, 8.0 V, 7.3 V, 6.0 V, and 2.7 V.**
- If the existing circuit does **not provide the specified voltages**, you **will modify it** so that it does.
- Also, you must make sure that the **power ratings of the resistors are adequate for the application** and **determine how long the battery will last with the voltage divider connected to it.**


Step 1: Drawing the Schematic of the Circuit

Use the Figure below to **determine the resistor values** and **draw the schematic of the voltage-divider circuit**. All the resistors on the board are **0.25 W**.
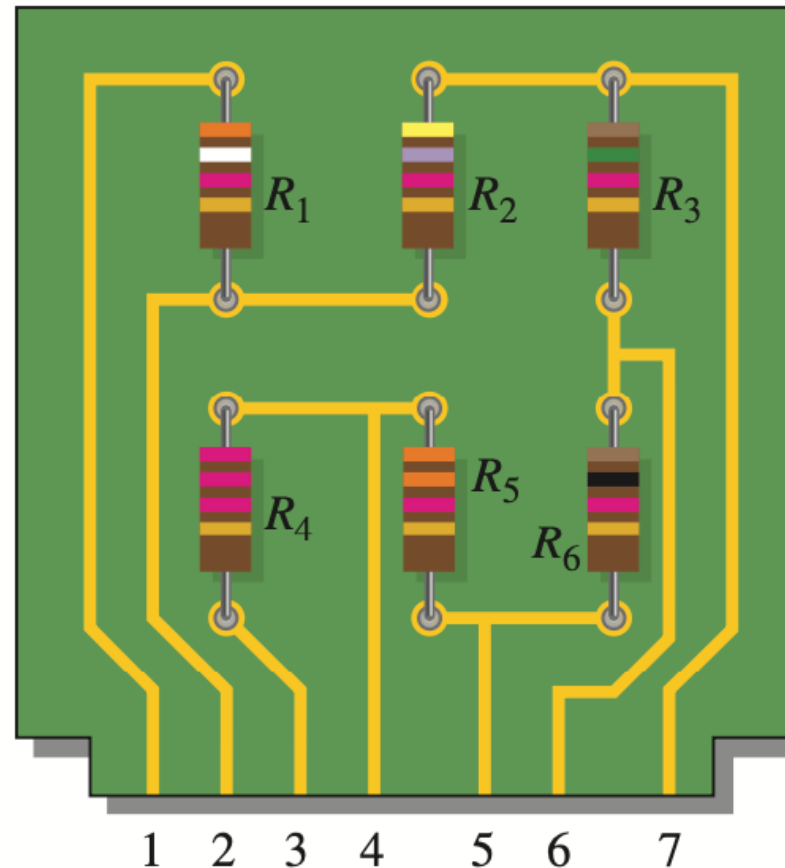
$$R_1 = 3.9 \text{ k}\Omega, R_2 = 4.7 \text{ k}\Omega, R_3 = 1.5 \text{ k}\Omega$$
$$R_4 = 2.2 \text{ k}\Omega, R_5 = 3.3 \text{ k}\Omega, R_6 = 1.0 \text{ k}\Omega$$



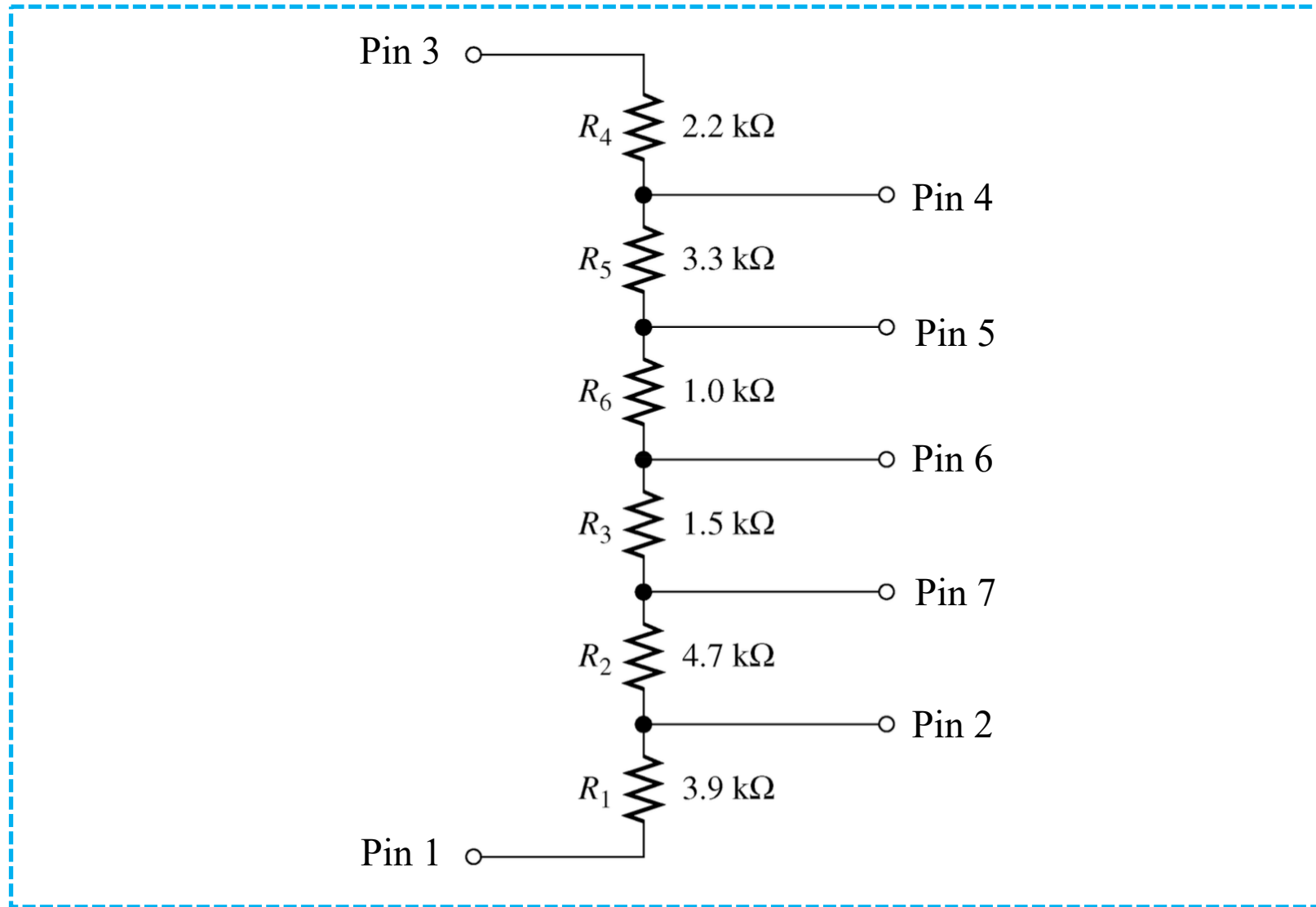Solution to Step 1: Drawing the Schematic of the Circuit



Step 2: Determining the Voltages

- Determine each output voltage on the existing circuit board when the positive side of the 12 V battery is connected to **pin 3** and the negative side is connected to **pin 1**.
- Compare the existing output voltages to the following specifications:

Pin 1: Negative terminal of 12 V battery

Pin 2: $2.7 \text{ V} \pm 5\%$

Pin 3: Positive terminal of 12 V battery

Pin 4: $10.4 \text{ V} \pm 5\%$

Pin 5: $8.0 \text{ V} \pm 5\%$

Pin 6: $7.3 \text{ V} \pm 5\%$

Pin 7: $6.0 \text{ V} \pm 5\%$

Solution to Step 2: Determining the Voltages

- The total resistance:

$$\begin{aligned} R_T &= R_1 + R_2 + R_3 + R_4 + R_5 + R_6 \\ &= 3.9 \text{ k}\Omega + 4.7 \text{ k}\Omega + 1.5 \text{ k}\Omega + 1.0 \text{ k}\Omega + 3.3 \text{ k}\Omega + 2.2 \text{ k}\Omega = 16.6 \text{ k}\Omega \end{aligned}$$

- Calculations of output voltages:

$$V_2 = \left(\frac{R_1}{R_T} \right) V_S = \left(\frac{3.9 \text{ k}\Omega}{16.6 \text{ k}\Omega} \right) 12 \text{ V} = \mathbf{2.82 \text{ V}} \qquad V_5 = \left(\frac{R_1 + R_2 + R_3 + R_6}{R_T} \right) V_S = \left(\frac{11.1 \text{ k}\Omega}{16.6 \text{ k}\Omega} \right) 12 \text{ V} = \mathbf{8.02 \text{ V}}$$

$$V_7 = \left(\frac{R_1 + R_2}{R_T} \right) V_S = \left(\frac{8.6 \text{ k}\Omega}{16.6 \text{ k}\Omega} \right) 12 \text{ V} = \mathbf{6.22 \text{ V}} \qquad V_4 = \left(\frac{R_1 + R_2 + R_3 + R_6 + R_5}{R_T} \right) V_S = \left(\frac{14.4 \text{ k}\Omega}{16.6 \text{ k}\Omega} \right) 12 \text{ V} = \mathbf{10.4 \text{ V}}$$

$$V_6 = \left(\frac{R_1 + R_2 + R_3}{R_T} \right) V_S = \left(\frac{10.1 \text{ k}\Omega}{16.6 \text{ k}\Omega} \right) 12 \text{ V} = \mathbf{7.30 \text{ V}}$$

- Are all voltages within 5% of specified values?

Yes

Step 3: Modifying the Existing Circuit (if necessary)

- If the **output voltages of the existing circuit are not the same** as those stated in the specifications of Step 2,
 - **Make the necessary changes** in the circuit to meet the specifications.
 - **Draw a schematic of the modified circuit** showing resistor values and adequate power ratings.

Solution to Step 3: Modifying the Existing Circuit (if necessary)

- Since the output voltages of the existing circuit **meet the specifications**, no resistor value changes are required.
- The **maximum power** occurs in R_2 .

$$I = \frac{12 \text{ V}}{R_T} = \frac{12 \text{ V}}{16.6 \text{ k}\Omega} = 723 \text{ }\mu\text{A}$$

$$P_{\max} = I^2 R_2 = (723 \text{ }\mu\text{A})^2 4.7 \text{ k}\Omega = \mathbf{2.46 \text{ mW}}$$

- The **0.25 W** rating of each resistor is **more than adequate**.

Step 4: Determining the Life of the Battery

- Find the total current drawn from the 12 V battery when the voltage-divider circuit is connected.
- Determine how many days the 6.5 Ah battery will last.

Solution to Step 4: Determining the Life of the Battery

- Find the total current drawn from the 12 V battery when the voltage-divider circuit is connected.

$$I = \frac{12 \text{ V}}{R_T} = \frac{12 \text{ V}}{16.6 \text{ k}\Omega} = 723 \text{ }\mu\text{A}$$

- Determine how many days the 6.5 Ah battery will last.

$$(723 \text{ }\mu\text{A})(h) = 6.5 \text{ Ah}$$

$$h = \frac{6.5 \text{ Ah}}{723 \text{ }\mu\text{A}} = 8990 \text{ h}$$

$$\text{Number of days} = \frac{8990 \text{ h}}{24 \text{ h/day}} = \mathbf{374.6 \text{ days}}$$



<https://www.cardsnacks.com/>